



ACADEMIC TEAM

 [/groups/YES.YU](https://www.facebook.com/groups/YES.YU)
yes.yarmouky.com

[fb.com/groups/yes.yu](https://www.facebook.com/groups/yes.yu)

Exp 2+3+4 :-

- $X_L = \omega L$
- $X_C = \frac{1}{\omega C}$ ← dependents of frequency

$R \Rightarrow$ Indep. of frequency


$$V_{rms} = \frac{V_p}{\sqrt{2}} = \frac{V_{p-p}}{2\sqrt{2}}$$

$$V_{p-p} = 2\sqrt{2} V_{rms}$$

$$V_p = \sqrt{2} V_{rms}$$

$$R = \frac{V_{p-p}}{I_{p-p}}$$

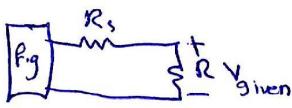
$$R_s \text{ given} \Rightarrow I = \frac{V_{given}}{R_s}$$



$$\text{given } V_{given} \Rightarrow X_C = \frac{V_{given}}{I_{p-p}}$$

$$\Rightarrow X_L = \frac{V_{p-p}}{I_{p-p}}$$

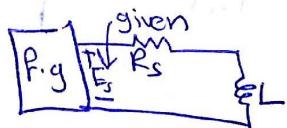\Rightarrow when $F \uparrow \Rightarrow X_L \uparrow \Rightarrow V_L \uparrow$



$$V_{source} = \sqrt{V_L^2 + V_R^2}$$

$\Rightarrow F \downarrow \rightarrow L$ short cct

$F \uparrow \rightarrow L$ open cct (high impedance)

E_s و مارجع اوقات حمل E_s $\leftarrow R-C \rightarrow RL$ \rightarrow E_s \leftarrow E_s \rightarrow E_s \leftarrow E_s \rightarrow E_s

Exp 5 :-

$\Rightarrow V, I, R$

in phase (→)


$\Rightarrow V, I, C$

out of phase \Rightarrow in R-C cct - I lead E_s by 90°

V_c lag E_s by 90°

$\Rightarrow V, I, L$

out of phase

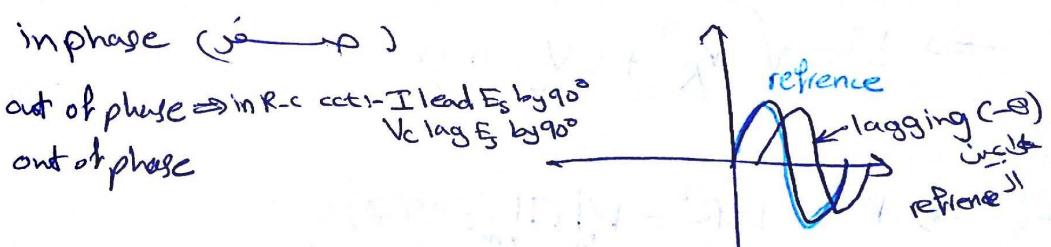


- two methods to measure phase:-

Dual trace


Lissajous (XY phase)

$$\text{SF : Scale factor} = \frac{360^\circ}{T_0} \quad (\text{degrees/division})$$
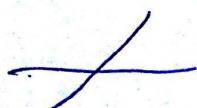
$$\theta = \frac{D_{signal}}{D_{reference}} \times 360^\circ$$



$$\theta = 0, 360^\circ$$

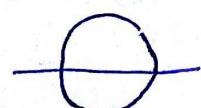

$$\theta = 270, 90^\circ$$




$$\theta = 180^\circ$$



$$\theta = \sin^{-1} \frac{Y_o}{Y_m}$$


(نیز اسکالر داشتیم)

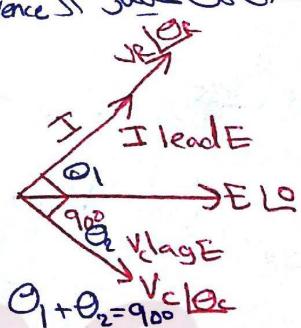

$$\theta = 180^\circ - \sin^{-1} \frac{Y_o}{Y_m}$$

(نیز اسکالر داشتیم)

R-C circuit:-

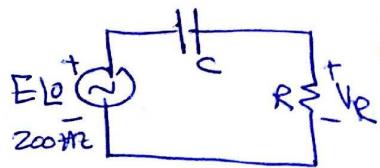

$$\frac{V_R}{R + jX_C} = \frac{E}{R + jX_C}$$

$\rightarrow V_R = \frac{ER}{R^2 + X_C^2}$

$$\theta_1 = \tan^{-1} \left(\frac{X_C}{R} \right)$$

magnitude.



$$V_C = \frac{EX_C}{R^2 + X_C^2}$$

$$\theta_2 = -90^\circ + \tan^{-1} \left(\frac{X_C}{R} \right)$$

مقدار الميل
أو زاوية التأخير

$$\% \text{ Diff} = \left| \frac{\text{Calculated}}{\text{Actual}} - \frac{\text{Measured}}{\text{Actual}} \right| \times 100\%$$

RLC circuit:-

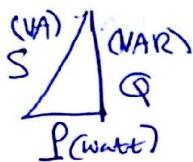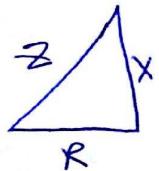

$$Z^2 = R^2 + X^2$$

$$Z = R + jX$$

RL circuit:-

I lags V by 90°

$$\Rightarrow E = \sqrt{V_R^2 + (V_L - V_C)^2}$$


$$\Rightarrow P = I^2 R^2 = |V_{rms}| |I_{rms}| \cos(\phi)$$

$\rightarrow \phi_V - \phi_I$

$$\Rightarrow Z_{tot} = \frac{E}{I} = (R - jX_C + jX_L) \frac{I}{I}$$


$$\Rightarrow I = \frac{E}{Z_{tot}}$$

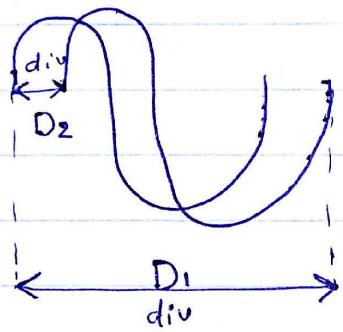ابرزد اینکه فیصله را در لامپ میتوان از جریان آن درآورد




$$\theta = \frac{D_2}{D_1} * 360$$

Lead + Lag -

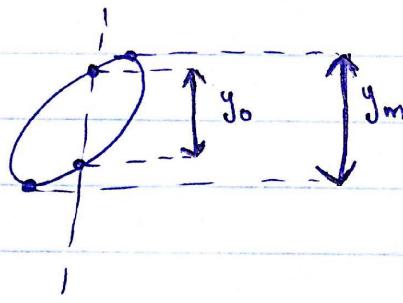
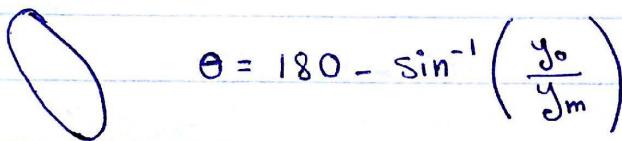
$$\theta = \sin^{-1} \left(\frac{y_0}{y_m} \right)$$



$$\theta = 180 - \sin^{-1} \left(\frac{y_0}{y_m} \right)$$


$$X_C = \frac{1}{2\pi f C_T}$$

$$X_L = 2\pi f L_T$$

$$\omega = 2\pi f$$

$$(P-p) = rms * 2\sqrt{2}$$


$$rms = \frac{P-p}{2\sqrt{2}}$$

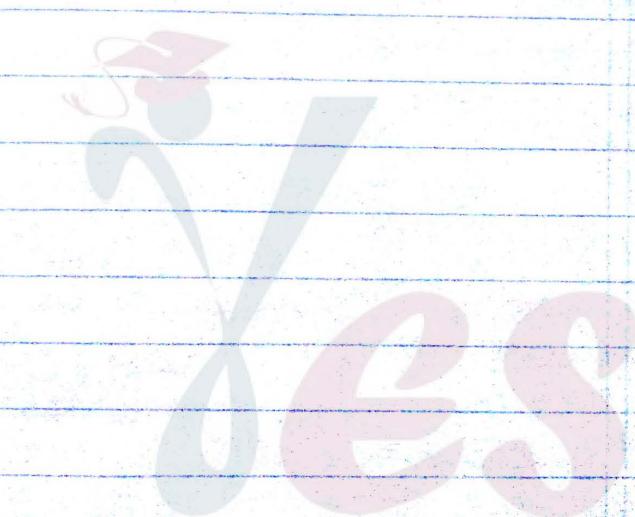

Name:

5
10

II) find the following:

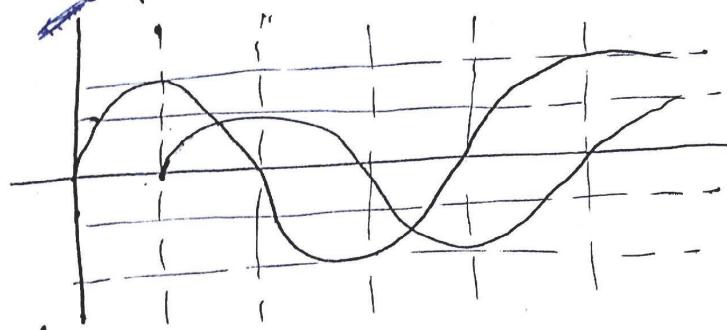

copy from
Naredu, Yasmeen
aysha

note that:

$$\text{Time } 1/\text{div} = 5 \text{ ms}$$

$$V_1 = 6 \text{ volt p-p}$$

$$V_2 = 3 \text{ volt p-p}$$

a) find the phase angle between the two signals in details: (4 marks)


b) name the two ways to find the phase angle: (2 marks)

① Dual-trace method.

② Lissajous - pattern

(4 marks)

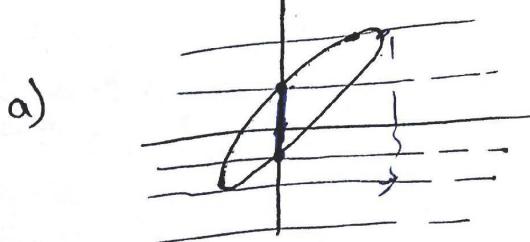II) determine the phase angle in the following figures:



$$\text{volt } 1/\text{div} = 3$$

$$\theta = \sin^{-1} \left(\frac{2}{4} \right) \Rightarrow \theta = 30^\circ$$

$$\sin^{-1} \left(\frac{2}{4} \right)$$

b)



$$\text{volt } 1/\text{div} = 2$$

$$\theta = 180 - \left(\sin^{-1} \left(\frac{1}{3} \right) \right)$$

$$= 180 -$$


$$\sin^{-1} ($$

Good Luck


Eng. Aseel H. Abu Albas

15%

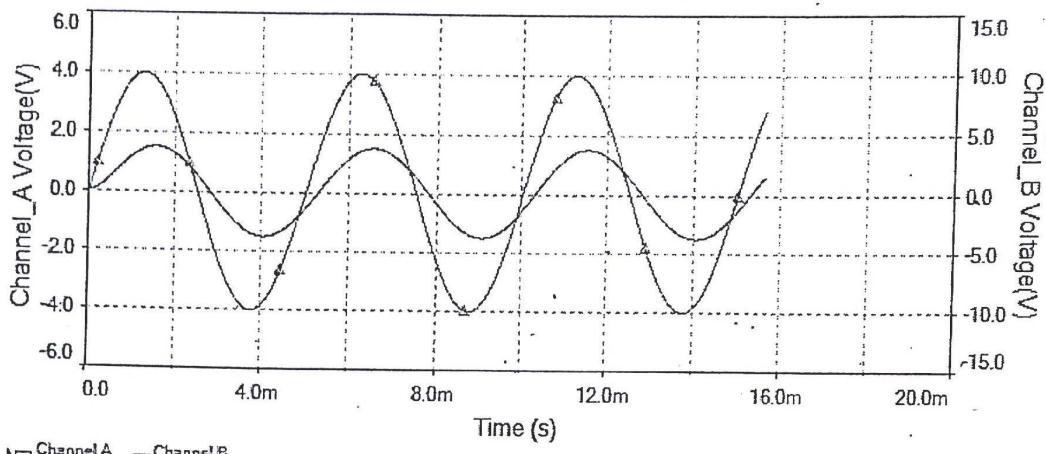Q1: Assume that the pattern in the following figures appear on an oscilloscope screen ,calculate the phase angle θ


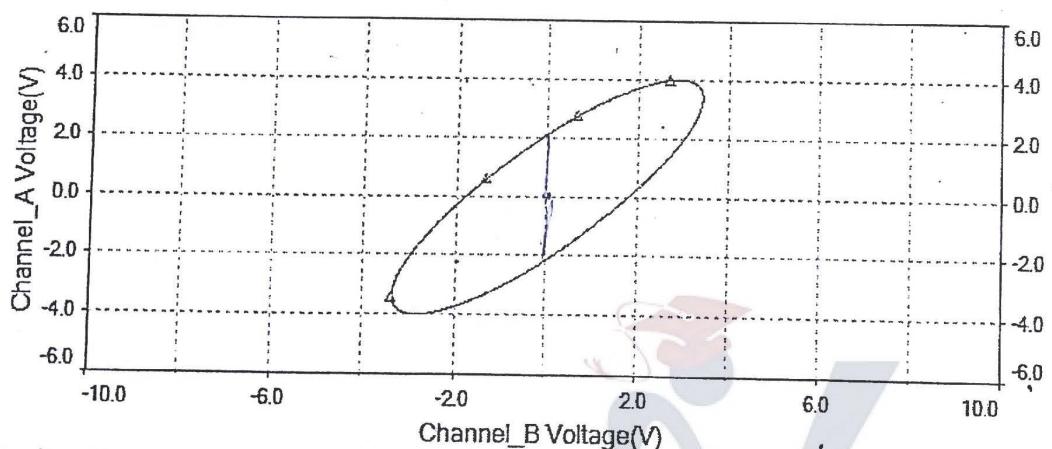
$$\theta = \sin^{-1} \frac{y_o}{y_m} = \sin^{-1} \left(\frac{2 \times 10^{-3}}{2.4} \right) = 0.0477^\circ \quad \text{X}$$



$$\theta = \frac{D_2}{D_1} 360^\circ = \frac{2}{4} 360^\circ = 180^\circ$$

$$D_2 = 2$$

$$D_1 = 4$$

Q2: Complete the table below if given that the Freq=500Hz and C=0.1μF

R	Xc	Θ
1000Ω	-j 31.63 · 1	✗
2000Ω	-j 31.63 · 1	✗
4000Ω	-j 31.63 · 1	✗

1.5

Q3: Draw the Lissajous-pattern phases for these ranges of Θ:
Θ=360

✗

Θ=90

✗

Θ=180


✗



(8/10)

Q1: Assume that the pattern in the following figures appear on an oscilloscope screen , calculate the phase angle θ


150

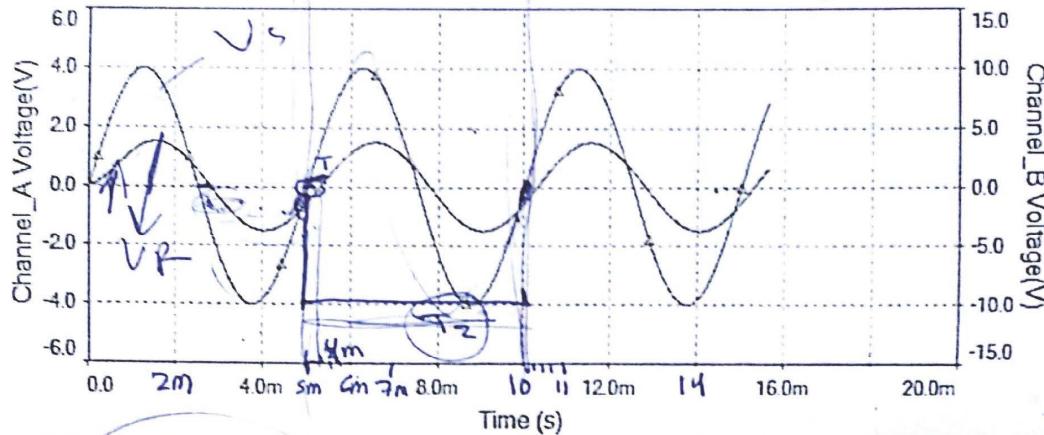

Channel A Channel B


$$\theta = \frac{T_{small}(1) \times 360^\circ}{T_{large}(2)} = \frac{4\text{ ms}}{5\text{ ms}} = \frac{0.4\text{ m}}{5\text{ m}} \times 360^\circ = 28.8^\circ$$

D₁ D₂ (2)

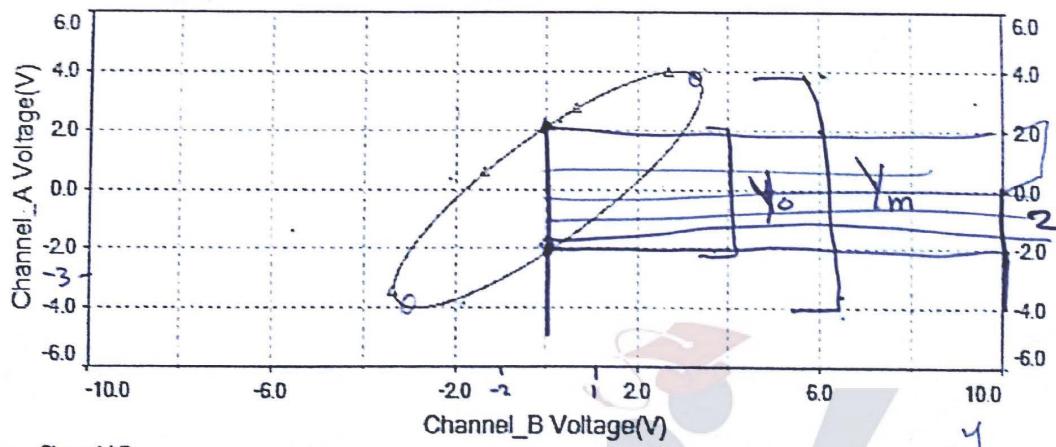

Channel A/B
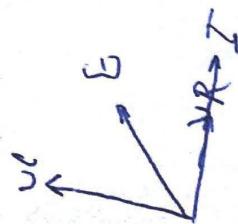
$$\theta = \tan^{-1} \left(\frac{Y_0}{X_m} \right) = \sin^{-1} \left(\frac{4.5}{8} \right) = 31.67^\circ$$



5. 1/25


Q2: Complete the table below if u given that the Freq=500Hz and
C=0.1μF

R	Xc	θ
1000Ω	$\frac{1}{2\pi fC} = 3183.1 \cancel{\Omega}$	$\tan^{-1}\left(\frac{X_C}{R}\right) = 72.56^\circ$
2000Ω	3183.1	57.86°
4000Ω	3183.1	38.5°



3

Q3: Draw the Lissajous-pattern phases for these ranges of Θ:
 $\Theta=360^\circ$


$\Theta=90^\circ, 270^\circ$

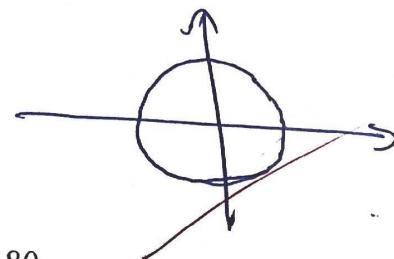

$\Theta=180^\circ$

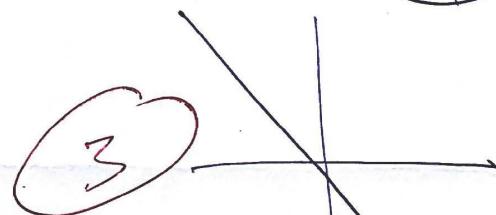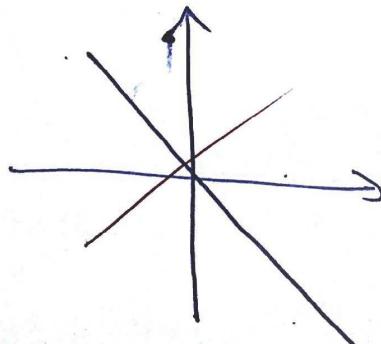


3

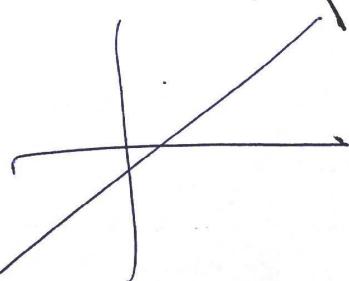

Yarmouk University
 Hijjawi Faculty for Technological Engineering
 Power Engineering Department
 Second Semester 2014
 Electric Circuit Lab__ Mid Exam

*****Note: You must show your calculations .*****

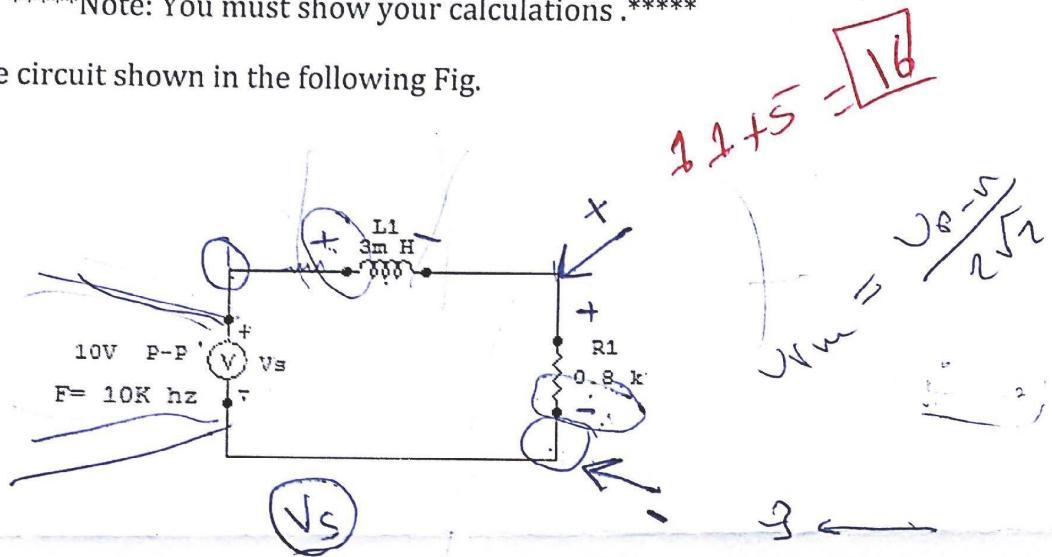Q.1 Construct the circuit shown in the following Fig.



*1. measure the following quantities :

$R_L = 5.3 \Omega$	$V_L(p-p) = 0.7 \times 2 \text{ V}$ $= 1.4 \text{ V}$	$V_R(0.8\text{k}) = 4.3 \times 2 \text{ V}$ $= 8.6 \text{ V}$	$I_{(\text{rms})} = 3.9 \text{ mA}$
--------------------	--	--	-------------------------------------

*2. Do V_R and V_L (increase or decrease or stay constant and Explain why ??

$F (\text{hz})$	10 K	15 K	20 K
$V_R \text{ rms}$	3.81	4.01	1.792
$V_L \text{ rms}$			

$$V_R \text{ (rms)} = \frac{V_R \text{ (p.p)}}{2\sqrt{2}} \rightarrow 3.81 \cdot \frac{8.6}{2\sqrt{2}} \rightarrow 3.81 \text{ V}$$

$$I_{\text{rms}} = \frac{3.81}{0.8} \text{ A}$$


*3. Measure the phase angle between Vs and VL (ONLY USE ONE METHOD):

*4..Find:

a.XL calculated :

b. XL measured (show all required measurements and calculations) :

$$X_L = 2\pi f L = 2 \pi$$

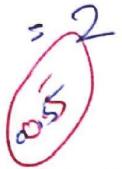

$$X_L = \frac{V}{I}$$

Best wishes

Eng. Asmaa Talal



ACADEMIC TEAM